

# Contents

<b>1 Lecture 1</b>	<b>1</b>
1.1 Volt calssification . . . . .	1
1.2 Electric circuits . . . . .	1
1.3 Basic circuit quantities . . . . .	2
1.4 Basic circuit analysis . . . . .	2
1.5 Basic circuit elements . . . . .	2
1.6 Basic circuit laws . . . . .	3
date: 13-2-23	

## 1 Lecture 1

### 1.1 Volt calssification

- up to 1000V » Low voltage
- between 1kV and 50kV » Mideum voltage
- between 50kV and 500kV » High voltage

### 1.2 Electric circuits

For the circuits to be a circuit it needs:

- A supply
- A load
  - Light
  - Heat
  - Mechanical energy aka a motor
- A wire
- A switch

### 1.3 Basic circuit quantities

Most common types of wire are copper (Cu) and aluminum (Al).

1. The charge ( $q > \text{coulumb}$ )

2. The current ( $I > \text{ampere} = \text{C/S}$ )

The rate of change of the quantity of charges.

$$I = \frac{dq}{dt} > \text{differentiation of the charge}$$

$$q = \int i(t).dt > \text{integration of the current}$$

Example:

$$q = 12e - 12t \rightarrow I = 12(-12)e - 12tmA$$

3. The potential difference ( $V > \text{volt} = \text{J/C}$ )

The energy affecting the charge to move it a certain distance.

$$V = \frac{dW}{dq}$$

4. The electrical energy ( $W > \text{joule}$ )

5. The electrical power ( $P > \text{watt} = \text{J/S}$ )

$$p = \frac{dW}{dt} = I \times V = V \times I = I^2 \times R = \frac{V^2}{R}$$

### 1.4 Basic circuit analysis

1. DC circuits

Constant voltage and current.

2. AC circuits

Alternating voltage and current.

### 1.5 Basic circuit elements

1. Passive elements

Elements that absorb the electrical energy.

- The most common passive elements:
  - The resistor ( $R > \text{ohm}$ ) (DC & AC)
  - The electrical coil ( $L > \text{henery}$ ) (AC only)
  - The capacitor ( $C > \text{farad}$ ) (AC only)

## 2. Active elements

Elements that generate the electrical energy.

### (a) Current source

Identified from the direction.

- Independant  
Constant current intensity.
- Dependant (Voltage controlled - $V_x$ - || Current controlled - $I_y$ -)  
Variable current intensity.

### (b) Voltage source

Identified from the polarity.

- Independant  
Constant voltage
- Dependant (Voltage controlled - $V_y$ - || Current controlled - $I_o$ -)  
Variable voltage

## 1.6 Basic circuit laws

### 1. Ohm's law

$$V = I \times R$$

- Power types (Conventional sign rule)  
Only applied when both the current and voltage are positive.
  - (a) Power absorbed  
Current enters the element from the positive side.
  - (b) Power supplied/delivered  
Current leaves the element from the positive side.

For any balanced circuit (with an ideal wire) the sum of the power consumed equals the sum of the supplied power

### 2. Kirchoff's law

[NEXT LECTURE]