

Thevinin's Theory


- Thevinin's theory states that in a circuit, all resistors can be replaced by one resistor that consumes the same amount of power and a voltage source series to it.
- In the "Thevinin" circuit, the positive pole of the source is connected to the resistor if E_{TH} is positive and vice versa.
- If a resistor is series with a current source, this resistor is not included in either nodal or mesh equations.

Cases

1. Independent source + Resistor
2. Independent source + Dependant source + Resistors
3. Dependant source + Resistors


Example

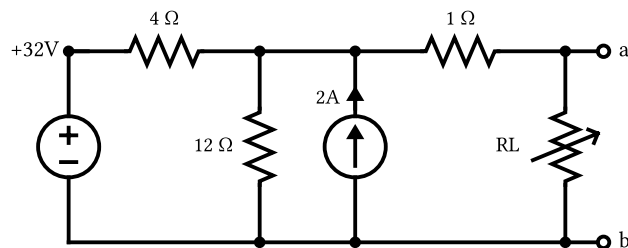1. (Case 1) Find thevenin's equivalent at the terminals a-b




Sol:

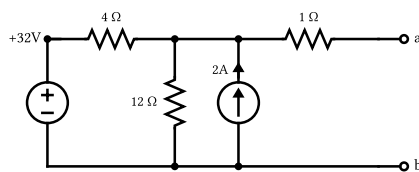1. Disconnect the element at which the quantity is required. (R_L)



2. Deactivate all sources.

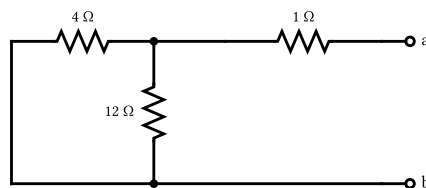


3. Calculate R_{TH}



$$R_{eq} = R_{TH} = \frac{4 \times 12}{4 + 12} + 1 = 4\Omega$$

4. Calculate E_{TH}

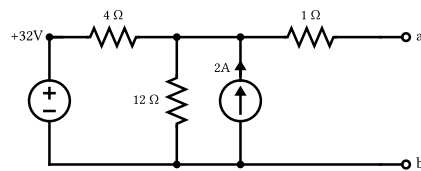


- Using Nodal analysis at V_1 (The node between 4 and 12Ω using 'b' as the ground):

$$2 = \frac{V_1 - 0}{12} + \frac{V_1 - 32}{4} \rightarrow V_1 = 30V$$

∴ No current is between a-b.


$$\therefore E_{TH} = V_1 = 30V$$

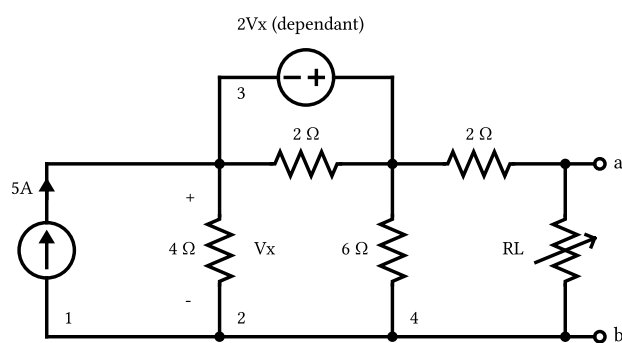2. (Case 2) Find thevenin's equivalent at the terminals a-b



Sol:

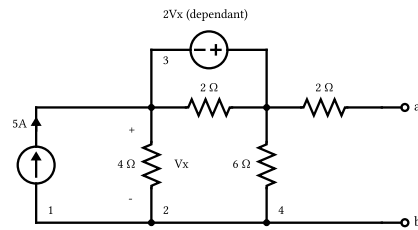1. Disconnect the element at which the quantity is required. (R_L)



2. Calculate E_{TH}

- Using Mesh analysis:

$$I_1 = 5A$$

Mesh equation for I_2 :


$$0 = I_2(4 + 6 + 2) - I_1(4) - I_3(2)$$

Mesh equation for I_2 :

$$2V_x = I_3(2) - I_2(2)$$

$$\therefore E_{TH} = 6 \times I_2$$

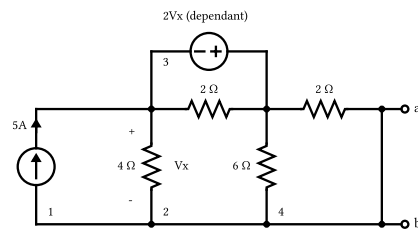3. Create a short circuit between a-b and calculate I_{ab}



- Using Mesh analysis:

$$I_1 = 5A$$

$$0 = I_2(4 + 6 + 2) - I_1(4) - I_3(2)$$

$$2V_x = I_3(2) - I_2(2) - I_4(6)$$

$$0 = I_4(2 + 6) - I_2(6)$$

$$V_x = 4(I_1 - I_2)$$

$$\therefore R_{TH} = \frac{V_{ab}}{I_{ab}}$$

Norton's theory

- Norton's theory states that in a circuit, all resistors can be replaced by one resistor that consumes the same amount of power and a current source parallel to it.

Examples

1. Find Norton's equivalent at the terminals a-b.

Sol:

1. Disconnect all sources.
2. Calculate R_N .

$$R_N = 6\Omega$$

3. Calculate $I_N = I_{ab}$.
 - Using nodal analysis:

$$0 = \frac{V_1 - 1}{6} + \frac{V_1 - 0}{3} + \frac{V_1 - 0}{10}$$

- Using KCL:

$$\frac{18 - 0}{12} + \frac{V_1 - 0}{10} = I_{ab}$$

4. Draw the "Norton" circuit.