

# Diodes

## Introduction

A diode is made of a semi-conductor between a conductor and an insulator (conductor - semi-conductor - insulator). Resistivity increases when going from right to left and vice versa.

## Doping

Doping is adding impurities to a material to change its properties. When silicon is doped with boron, the positive charges of silicon are more than the negative charges (P-type). However when silicon is doped with phosphorous, the negative charges are more than the positive charges (N-type).

## Diode (The non-linear element)

A diode is the combination of a P-type and an N-type with a depletion region in between.

Connecting the diode to a battery of voltage  $V_s$  able to break the depletion region leads to a current passing from the P-type side to the N-type side.

Diodes act like a closed switch when (Forward mode):

$$V_a > V_k V_{ak} > V_{Do}$$

(a → anode, k → cathode,  $V_{Do}$  → depletion breaking voltage)

and an open switch when (Reverse mode):

$$V_a < V_k V_{ak} < V_{Do}$$

Therefore the current passing through a diode:

$$I = I_s \left( e^{\frac{V}{\eta V_T}} - 1 \right)$$

“ $\eta$ ” is the ideality factor of the diode. “ $I_s$ ” is the reverse saturation current passing through the diode in the reverse mode (Theoretically equals zero). “ $V_T$ ” is the thermal voltage which is the voltage affected by heat.

$$V_T = \frac{kT}{q}$$

Where T is the temperature, k is the boltzman constant and q is the electron charge.

## Diode (Electronic Valve) Models

1. Ideal model
2. Approximate model
3. Actual model

### Ideal model

In an ideal model, in a forward connection the diode is replaced by a closed switch and by an open switch in a reverse connection.

### Approximate model


In an approximate model, in a forward connection the diode is replaced by a battery of voltage ranging between 0.3V and 0.7V and by an open switch in a reverse connection.

## Actual model

In an actual model, in a forward connection the diode is replaced with a battery of voltage  $V_{D0}$  series with a resistance of  $r$  and by an open switch in a reverse connection.
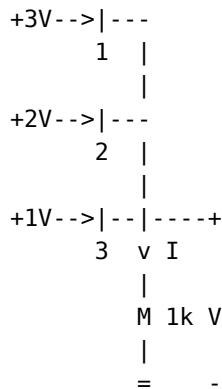
## Examples

- Find  $V$  and  $I$  in the opposite circuit.




sol:

- Assume that the diode with the most voltage is the 'on' diode.

$$\therefore V = 3V$$


$$\therefore I = \frac{3}{1000} \text{ mA}$$

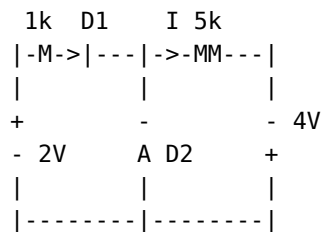- Find " $I$ " assuming an approximate model ( $V_{D0} = 0.6V$ )



sol:

- Assume both diodes are on:

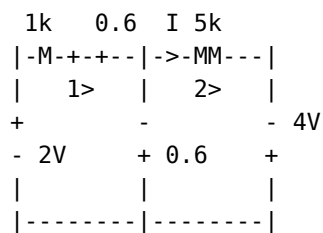

Using mesh analysis: mesh 1:

$$2 - 0.6 + 0.6 = I_1(1)$$

$$\therefore I = 2\text{mA}$$


mesh 2:

$$-0.6 + 4 = I_2(5)$$

$$\therefore I_2 = 0.68\text{mA}$$

2. Using the directions of the currents obtained:

$D_1$  is on while  $D_2$  is off.

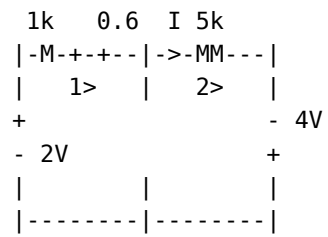

Using KVL:

$$0 = 2 + I + 0.6 + 5I - 4$$


$$\therefore I =$$

## Diode Applications

### The Rectifier Circuit

The rectifier circuit converts the AC to a DC.

1. Half Wave Rectifier

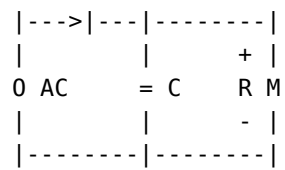

2. Full Wave Rectifier

TODO

The DC from FWR > DC from HWR